

# Manual for setting up the sensors of the Monitoring Box

Mick Nieman  
Amsterdam University of Applied Sciences

Pjotr Scholtze  
Amsterdam University of Applied Sciences

Heeyeon Joung  
Seoul National University of Science and Technology

November 2017

### **Abstract**

This has not been written yet and still needs content to be placed here.

# Contents

1	Introduction	2
2	Requirements	3
3	Glossary	5
4	Pushing code to an Arduino Nano	6
5	Global Positioning System (GPS) sensor	7
6	Temperature and humidity sensor	9
7	Heartrate sensor	11
8	Regular carbon dioxide (CO <sub>2</sub> ) sensor	13
9	Advanced carbon dioxide (CO <sub>2</sub> ) sensor	15
10	Raspberry Pi Camera	17
11	Galvanic skin response sensor	18
12	Development issued example sensor	20
13	Development issued unknown sensor	21

# Chapter 1

## Introduction

# Chapter 2

## Requirements

For every sensor added there is need for an Arduino Nano. The Arduino Nano is a programmable microprocessor. Advanced users may be able to connect multiple sensors to a single Arduino Nano, note that this requires advanced knowledge of the communication protocols between the Raspberry Pi 3 b+ and Arduino Nano. Along with every Arduino Nano you need an USB A to Mini-USB B cable.

The first item needed for the GPS sensor is the Global Positioning System (GPS) module. We have used the Digilent 410-237 GPS-receiver board.

For the temperature and humidity sensor we have used the DHT22 module, this is a digital temperature- and humidity sensor. the DHT22 is more accurate (0,5° accuracy) than the previous, DHT11. It has a temperature reach from -40 to +80 °C. and has a humidity reach from 10% to 90% with an accuracy of 2,0 %.

The heart rate sensor consists of the MAXREFDES117# Reference Design Board with optical heart rate and pulse-oximetry monitor. It has integrated Red and Infrared LEDs. This works best on a person's fingertip or earlobe.

The CO<sub>2</sub> sensor comes in two varieties, the regular sensor which is affordable but less accurate and the advanced which has a higher costs and comes with higher accuracy.

The 'Regular CO<sub>2</sub> sensor' uses the MIKROE-1630 Daughter Board from Air Quality Click. It's an MQ-135 High sensitivity air quality sensor and potentiometer.

The 'Advanced CO<sub>2</sub> sensor' uses CO2meter.com its K-30 sensor. The K-30 sensor is an accurate gas sensor sensing up to 5000ppm (CO<sub>2</sub>) with an accuracy of 3%. Note that the advanced CO<sub>2</sub> meter does not work on the Arduino Nano and is only tested on the Arduino Uno.

The raspberry Pi Cam doesn't require to be connected to an Arduino and

can be plugged directly in to the Raspberry Pi its camera-port. For this project we used Sony's IMX219 8-Megapixel Pi Camera Board. It is able for taking photographs of 3280x2464 pixels or video's at 1080p at 30 frames per second.

The galvanic skin response sensor, or short GSR, measures the galvanic skin response based on the electrical conductance of the skin. For the Monitoring Box we have used the Grove-GSR sensor from seeed studio.

Every sensor has it's own schematics for assembling the sensors, the code running on the sensor can be downloaded from <https://github.com/pjotrscholtze/MonitoringBox>, for the exact link for a particular sensor see further into this document.

## Chapter 3

# Glossary

GND pin - Ground pin  
A1 pin - Analog pin 1

## Chapter 4

# Pushing code to an Arduino Nano



## Chapter 5

# Global Positioning System (GPS) sensor

The Global Positioning System(GPS) sensor, from now on called the GPS sensor, is named PmodGPS. The schematics for the assembly of the sensor are as follows.

 


Figure 5.1: Global Positioning System Schematics

Note that the actual sensor looks quite different, though the pinout is the same.

The actual sensor looks like the following:

 


Figure 5.2: GPS sensor

- 'VCC3V3' of the GPS sensor goes to the 5V(or VCC) of the Arduino,
- 'GND' of the GPS sensor goes to the GND of the Arduino,
- 'RXD' of the GPS sensor goes to D5 pin(TXD) of the Arduino
- 'TXD' of the GPS sensor goes to D6 pin(RXD) of the Arduino.

Downloading the code from <https://github.com/pjotrscholtze/MonitoringBox> and uploading the code to the Arduino Nano should result in a functional GPS sensor.

## Chapter 6

# Temperature and humidity sensor

The Temperature and humidity sensor is named 'DHT22' and 'AM2302'. The schematics for the assembly of the sensor are as follows.

 


Figure 6.1: Temperature and humidity Schematics

Below is the picture of explaining pin on the DHT22

 


Figure 6.2: Temperature and humidity sensor

There is no pin name on the sensor, so you need to see the order in which the pins are listed. When looking at the sensor in front, I'll call the leftmost pin 'pin1'.

- 'pin 1' of the Temperature and humidity sensor(VCC) goes to the 5V(or VCC) of the Arduino,
- 'pin 2' of the Temperature and humidity sensor(DATA) goes to the D2 of the Arduino,
- 'pin 3' of the Temperature and humidity sensor is nothing. You do not need to connect anything.
- 'pin 4' of the Temperature and humidity sensor(GND) goes to GND of the Arduino.

Downloading the code from <https://github.com/pjotrscholtze/MonitoringBox> and uploading the code to the Arduino Nano should result in a functional Temperature and humidity sensor.

## Chapter 7

# Heartrate sensor

The Heart-rate sensor which is a sensor developed by Maxim integrated is named MAXREFDES117#. The schematics for the assembly of the sensor are as follows.

 


Figure 7.1: Heart rate Schematic

Note that the actual sensor looks quite different, though the pinout is the same.

The actual sensor looks like the following:

 


Figure 7.2: Heart rate sensor

- 'VIN' of the Heartrate sensor goes to the 5V(or VCC) of the Arduino,
- 'GND' of the Heartrate sensor goes to the GND of the Arduino,
- 'SDA' of the Heartrate sensor goes to A4 pin(SDA) of the Arduino
- 'SCL' of the Heartrate sensor goes to A5 pin(SCL) of the Arduino.

In Arduino-nano that we used doesn't have SDA and SCL name on the arduino. However, A4 and A5 act as SDA and SCL, respectively. If your Arduino has an SDA or SCL pin, you can connect it by name.

Downloading the code from <https://github.com/pjotrscholtze/MonitoringBox> and uploading the code to the Arduino Nano should result in a functional GPS sensor.

For more information about this sensor, Please visit below website.

<https://www.maximintegrated.com/en/design/reference-design-center/system-board/6300.html>

# Regular carbon dioxide (CO<sub>2</sub>) sensor

The regular carbon dioxide (CO<sub>2</sub>) sensor, from now on called the regular (CO<sub>2</sub>) sensor, is a sensor developed by mikroelektronics, and the schematics for the assembly of the sensor are as follows.

 


Figure 8.1: Air Quality Click Schematic

Note that the actual sensor looks slightly different, though the pinout is the same, the 5.5V pin of the Air-quility-click goes onto the 5.5V pin on the Arduino, the GND pin on the Air-quility-click goes onto the GND pin on the Arduino and the OUT pin on the Air-quility-click goes onto the A1 pin of the Arduino.

The actual sensor looks like the following:



Figure 8.2: The MikroE Gas Detector

The code coming with this sensor can be downloaded with the following link:  
[https : //github.com/pjotrscholtze/MonitoringBox/tree/develop/Sensors/CO2\\_Sensor](https://github.com/pjotrscholtze/MonitoringBox/tree/develop/Sensors/CO2_Sensor)

Downloading the code and uploading this to the Arduino Nano and having it assembled as the schematics show should result in a functional sensor.



## Chapter 9

# Advanced carbon dioxide (CO<sub>2</sub>) sensor

For starters, this CO<sub>2</sub> sensor is a little bit more complex than the other CO<sub>2</sub> sensor from the previous chapter. This sensor is more accurate but also works in a different way and not only the accuracy is higher, so is the price. The CO<sub>2</sub> sensor is developed by CO2meter.com and currently we're using the K30 model. During our testing phase we discovered that the K30 model is not compatible with the Arduino Nano nor with the Arduino Pro Mini but it is compatible with the Arduino UNO.

 


Figure 9.1: The K30 CO<sub>2</sub> sensor from CO2meter.com

After assembling the pins the right way, note that the pins on the K30 aren't labeled, but you will have to attach them to the inner (second) row, skipping the first pin, so using pin 2, 3, 4 and 5 from right to left.

- 'pin 2' of the K30 goes to the GND of the Arduino,
- 'pin 3' of the K30 goes to the 5V (or VCC) of the Arduino,

- 'pin 4' (the RXD pin) of the K30 goes to pin 12 (TXD) of the Arduino
- 'pin 5' of the K30 (TXD) goes to pin 13 (RXD) of the Arduino.

Downloading the code from <https://github.com/pjotrscholtze/MonitoringBox> and uploading the code to the Arduino UNO (this works the same way as with the Arduino Nano) should result in a functional CO<sub>2</sub> sensor.

## Chapter 10

# Raspberry Pi Camera

## Chapter 11

# Galvanic skin response sensor

Galvanic skin response sensor(GSR) sensor, from now on called the GSR sensor, does not require any sensor hardware. Only a little resistance is needed for stability. The schematics for the assembly of the sensor are as follows.

 


Figure 11.1: Galvanic skin response Schematic

The two current-carrying wires are connected to A0 and 5V, respectively, of

the Arduino. The resistors for stability are connected to A0 and GND respectively.

The way to use this GSR sensor is to put two fingers on two wires. Individual currents are different and will vary depending on emotional state or condition. To compare this, the result of the sensor will show the minimum, maximum and average values of the current. An example of usage and an example of the result value are shown in the following photograph.

## Chapter 12

# Development issued example sensor

## Chapter 13

# Development issued unknown sensor